

CprE 3810: Computer Organization and Assembly-Level Programming


Project Part 1 Report

Team Members: Luke Olsen, Matthew Estes

Project Teams Group #: A_02

Refer to the highlighted language in the project 1 instruction for the context of the following questions.

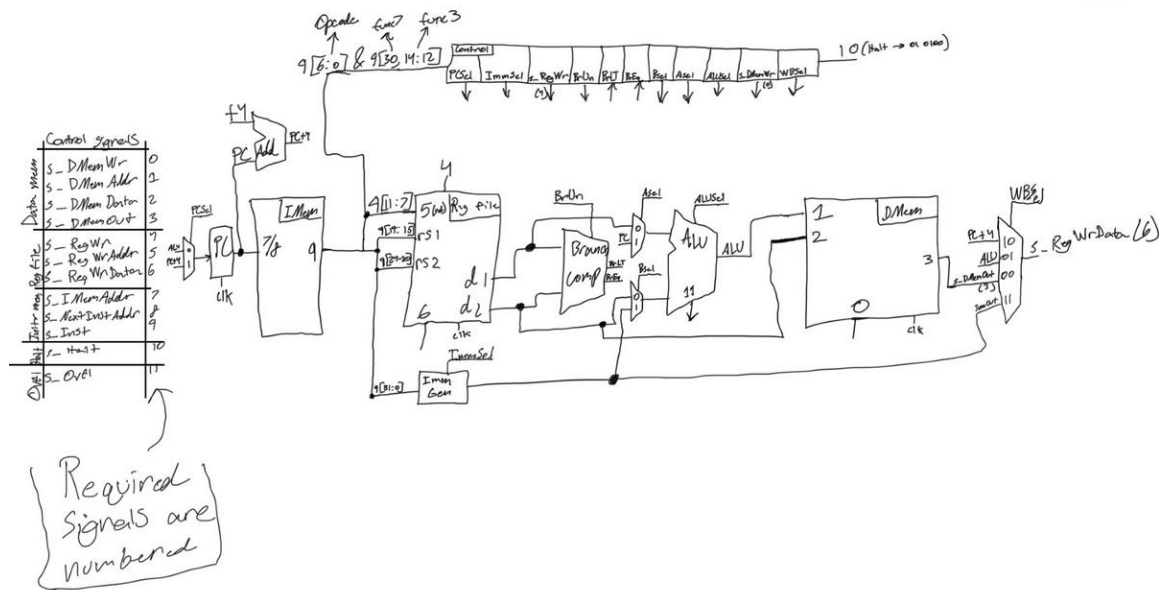[Part 2 (d)] Include your final RISC-V processor schematic in your lab report.




Note: The BrLt and BrEq are internal signals of the branch comp unit. They are not used as inputs or outputs but are there to help know what's going on inside the branch comp unit.

[Part 3.1.a.] Create a spreadsheet detailing the list of M instructions to be supported in your project alongside their binary opcodes and funct fields, if applicable. Create a separate column for each binary bit. Inside this spreadsheet, create a new column for the N control signals needed by your datapath implementation. The end result should be an $N \times M$ table where each row corresponds to the output of the control logic module for a given instruction.

	A	B	C	D	E	F	G	H	I	J	K
1	Instr	Opcode	ImmSel	s_RegWr	BrUn	Asel	Bsel	s_DMemV	WBSel	s_HALT	BR
2	add	110011	0	1	0	0	0	0	1	0	0
3	addi	10011	1	1	0	0	1	0	1	0	0
4	and	110011	0	1	0	0	0	0	1	0	0
5	andi	10011	1	1	0	0	1	0	1	0	0
6	lui	110111	100	1	0	0	1	0	11	0	0
7	lw	11	1	1	0	0	1	0	0	0	0
8	xor	110011	0	1	0	0	0	0	1	0	0
9	xori	10011	1	1	0	0	1	0	1	0	0
10	or	110011	0	1	0	0	0	0	1	0	0
11	ori	10011	1	1	0	0	1	0	1	0	0
12	slt	110011	0	1	0	0	0	0	1	0	0
13	slti	10011	1	1	0	0	1	0	1	0	0
14	sltiu	10011	1	1	0	0	1	0	1	0	0
15	sll	110011	0	1	0	0	0	0	1	0	0
16	srl	110011	0	1	0	0	0	0	1	0	0
17	sra	110011	0	1	0	0	0	0	1	0	0
18	sw	100011	11	0	0	0	1	1	0	0	0
19	sub	110011	0	1	0	0	0	0	1	0	0
20	beq	1100011	11	0	0	1	0	0	0	0	1
21	bne	1100011	11	0	0	1	0	0	0	0	1
22	blt	1100011	11	0	0	1	0	0	0	0	1
23	bge	1100011	11	0	0	1	0	0	0	0	1
24	bltu	1100011	11	0	1	1	0	0	0	0	1
25	bgeu	1100011	11	0	1	1	0	0	0	0	1
26	jal	1101111	101	1	0	1	1	0	10	0	0
27	jalr	1100111	1	1	0	0	1	0	10	0	0
28	lb	11	1	1	0	0	1	0	0	0	0
29	lh	11	1	1	0	0	1	0	0	0	0
30	lbu	11	1	1	0	0	1	0	0	0	0
31	lhu	11	1	1	0	0	1	0	0	0	0
32	slli	10011	1	1	0	0	1	0	1	0	0
33	srli	10011	1	1	0	0	1	0	1	0	0
34	srai	10011	1	1	0	0	1	0	1	0	0
35	auipc	10111	100	1	0	1	1	0	1	0	0
36	wfi	1110011	0	0	0	0	0	0	0	1	0

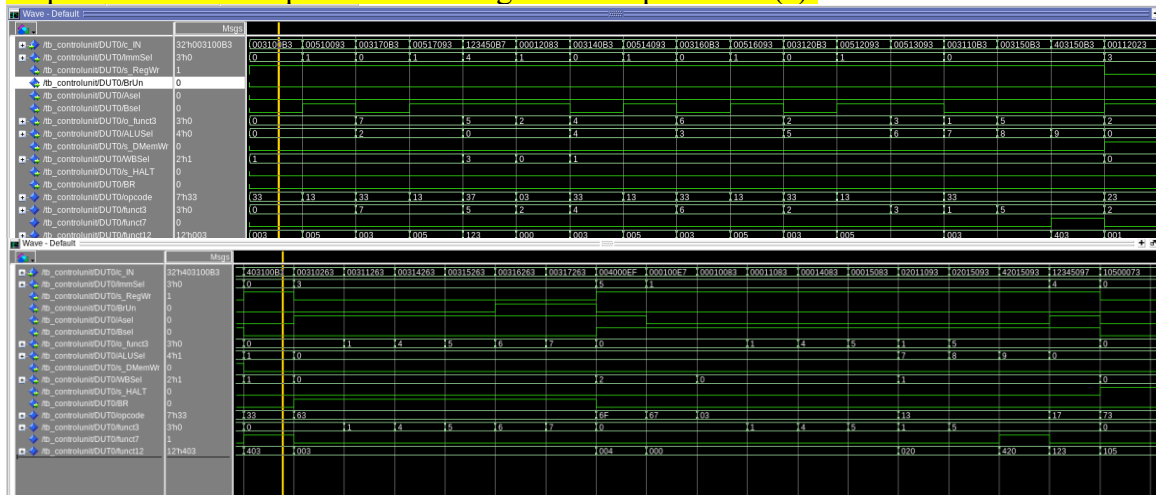
[Part 3.1.(b)] Implement the control logic module using whatever method and coding style you prefer. Create a testbench to test this module individually and show that your output matches the expected control signals from problem 1(a).



[Part 3.2. (a)] What are the control flow possibilities that your instruction fetch logic must support? Describe these possibilities as a function of the different control flow-related instructions you are required to implement.

For normal instructions, the fetch logic just increments $pc + 4$ to get the next instruction. For branch instructions, the pc must be added with the immediate value. For jump instructions like jal or $jalr$ the pc must be updated with a target address that comes from either the immediate value or a register. For jump and link the fetch logic also needs to store the return address into a register for safe keeping.

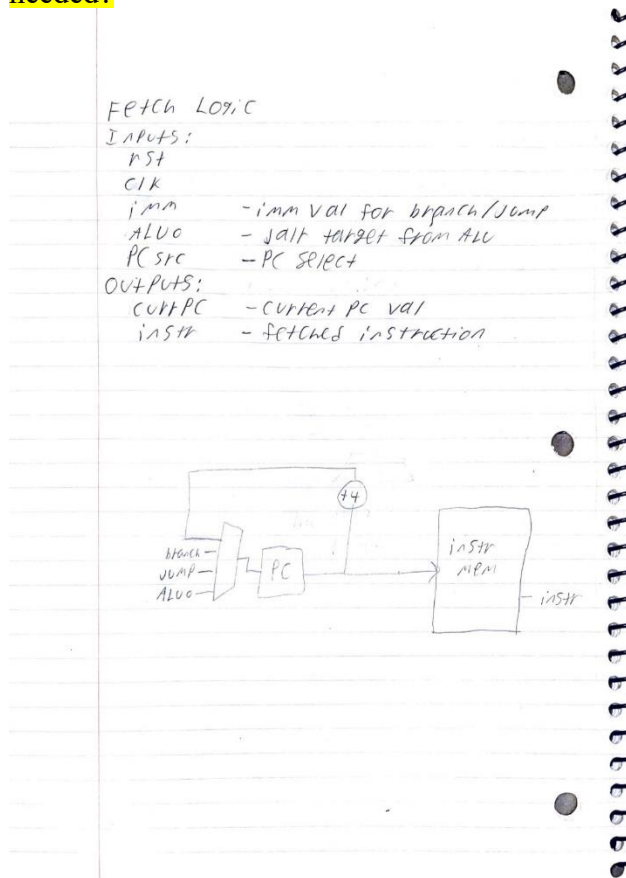
[Part 3.2. (b)] Draw a schematic for the instruction fetch logic and any other datapath modifications needed for control flow instructions. What additional control signals are needed?



[Part 3.2.(c)] Implement your new instruction fetch logic using VHDL. Use QuestaSim to test your design thoroughly to make sure it is working as expected. Describe how the execution of the control flow possibilities corresponds to the QuestaSim waveforms in your writeup.

Test 1


When $PCsrc = "00"$, the PC increments normally by 4 each clock cycle ($PC_next = PC + 4$), representing sequential instruction fetch.

 

Test 2

When PCsrc = "01", the ALU selects the branch target (PC + imm).


In the waveform, you'll see PC jump forward by 16 bytes.

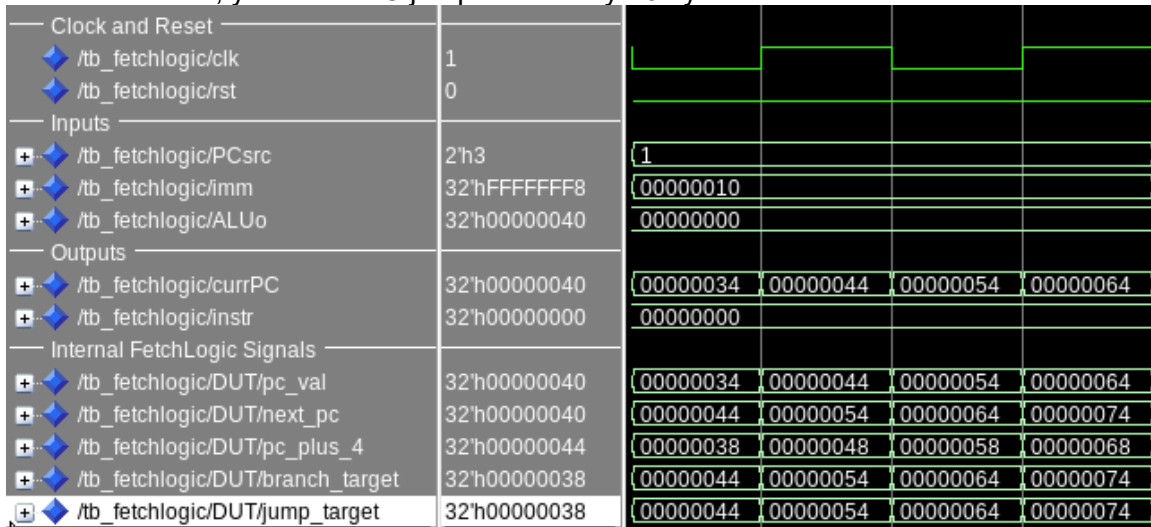

Test 3

or PCsrc = "10", the PC performs a jump using the immediate offset (PC + imm).


Since imm is negative, the waveform shows the PC jumping backward by 8 bytes (two instructions).

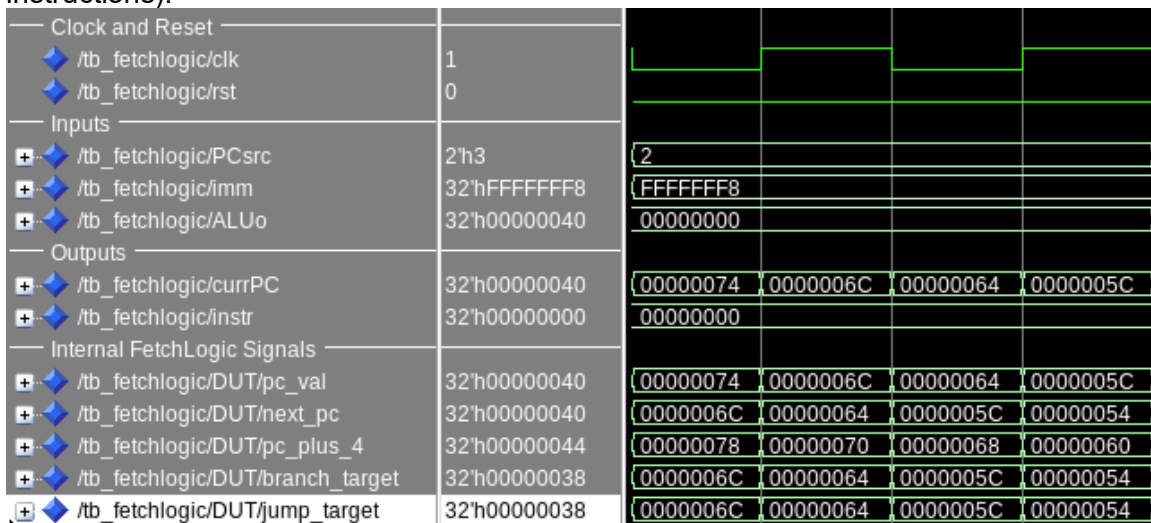

Test 4

When PCsrc = "11", the PC loads directly from the ALU output (PC_next = ALUo), which corresponds to JALR.

In the waveform, the PC jumps immediately to address 0x00000040, confirming that the absolute jump path functions correctly.

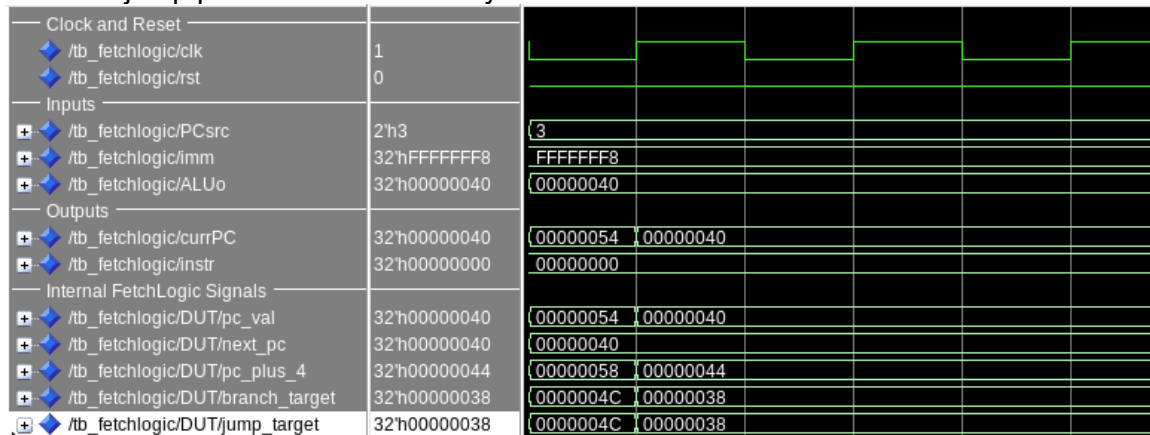

[Part 3.3.1.(a)] Describe the difference between logical (srl) and arithmetic (sra) shifts. Why does RISC-V not have a sla instruction?

- SRL: Logical shifts are better for unsigned values. Logical shifts shift the entire value for any value. This is good for multiplying and dividing values.
- SRA: Better for signed values. Arithmetic shifts keep the signed value of the number, a type of extension.


[Part 3.3.1.(b)] In your writeup, briefly describe how your VHDL code implements both the arithmetic and logical shifting operations.

The structural 32 bit right shifter is made using a generate statement to make 32 muxes. We then wire them to the corresponding neighbors based on the corresponding shift creating the cascading affect. The arithmetic and logical shifts are controlled by the i_ARI control signal. For logical zeros are shifted into the MSBs. For arithmetic shifts we shift the sign bit as the “fill bit”.

[Part 3.3.1.(c)] In your writeup, explain how the right barrel shifter above can be enhanced to also support left shifting operations.

Adding left shift support we use i_DIR to control the direction. For left shifts the bits are flipped or “reversed”. This way we don’t need to implement an entire second left shifter to perform the same thing.

 [Part 3.3.1.(d)] Describe how the execution of the different shifting operations corresponds to the QuestaSim waveforms in your writeup.




Test 1: Logical Left Shift. Test 2: Logical Right Shift. Test 3: Arithmetic right shift sign=1. Test 4: Arithmetic right shift sign=0. Test 5: Logical Left Shift edge case. Test 6: Logical right shift edge case. Test 7: Arithmetic right shifted edge case. Test 8: Zero input. Test 9: Pattern Test.

[Part 3.3.2.(a)] In your writeup, briefly describe your design approach, including any resources you used to choose or implement the design. Include at least one design decision you had to make.

Our design approach was to try to compact everything into blocks to make it easier to read and to make it more organized. One way to help was to separate the branch logic from the ALU into its own block.

 [Part 3.3.2.(b)] Describe how the execution of the different operations corresponds to the QuestaSim waveforms in your writeup.



The branch comp will output a signal of 1 signaling it is a branch being executed and the BrUn will indicate if its signed or unsigned.

[Part 3.3.3] Draw a simplified, high-level schematic for the 32-bit ALU. Consider the following questions: How is Zero calculated? How is `slt` implemented?

ALU

signals:


A - Data input 1

B - Data input 2

ALU Ctrl - tells the ALU what instruction

Result

Zero

 

Zero is calculated by looking at the result value and seeing if it is all 0's.


slt compares two signed integers and sets the result to 1 if $A < B$, otherwise 0.

[Part 3.3.5] Describe how the execution of the different operations corresponds to the QuestaSim waveforms in your writeup.

TESTBENCH INPUTS		
/tb_alu/i_A	32'h7FFFFFFF	00000005
/tb_alu/i_B	32'h00000004	0000000A
/tb_alu/Ctrl	4'h9	0 1
DUT INTERNALS		
/tb_alu/DUT/ALUctrl	4'h9	0 1
/tb_alu/DUT/A	32'h7FFFFFFF	00000005
/tb_alu/DUT/B	32'h00000004	0000000A
DUT OUTPUTS		
/tb_alu/ALU_Result	32'h07FFFFFF	0000000F FFFFFFFB
/tb_alu/o_zero	0	


When the Ctrl signal is set to "0000", the ALU is expected to perform an addition operation. In this test case:

$i_A = x"00000005"$

 

Proj1 base test screenshot^^initialization instructions

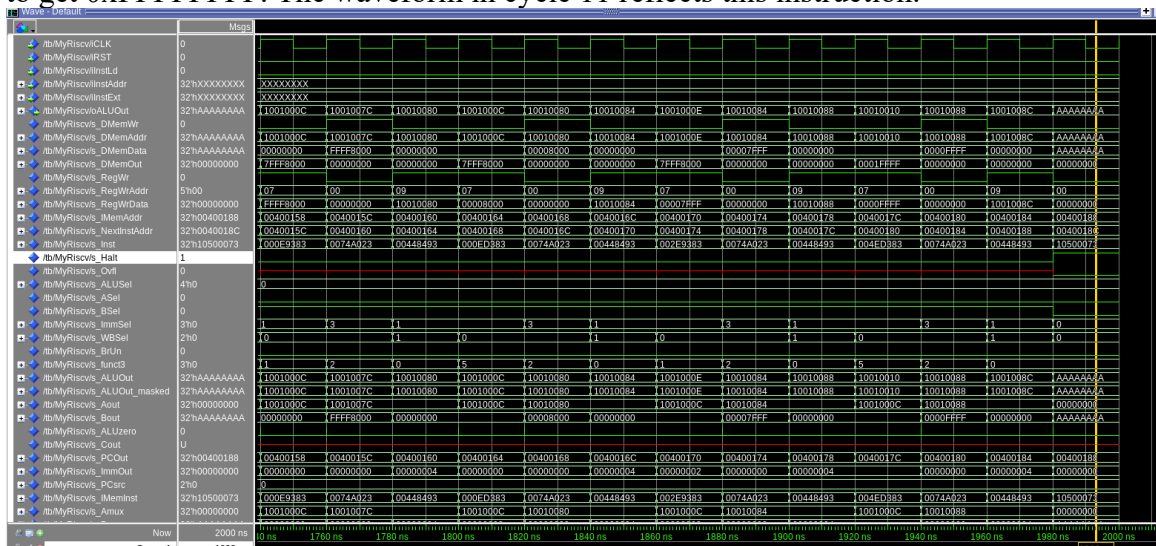This screenshot contains the initial instructions and initializations for the base test. We know this has correctness due to the waveforms matching the RISC-V test codes. For example: in cycle 11 we are adding $t0$ and $t1 \rightarrow 0xAAAAAAAA + 0x55555555$ together to get $0xFFFFFFFF$. The waveform in cycle 11 reflects this instruction.



At the end of the test we trigger the `s_Halt` signal which recognizes the 1110011 Halt opcode from the RISC-V ISA.

[Part 4.b] Create and test an application which uses each of the required control-flow instructions and has a call depth of at least 5 (i.e., the number of activation records on the stack is at least 4). Name this file `Proj1_cf_test.s`.

Opcode func7 func3

